

# CA3 VHDL(System on Chip (SoC))

Amirhossein ilkhani  
University of Tehran  
Tehran, Iran  
hossein.ilkhani1376@gmail.com

*System on Chip is an integrated circuit that integrates multiple components including digital, analog, hardware, and software programs in a single chip. The main component in an SoC is a processor for handling different computational tasks within the system.*

## A. SOC

Our system includes the main processor (PUNEH), FIR, DMA controller, Arbiter, and Programmable interrupt controller. The processor fills the coefficient registers and then set the DMA. After this with an in fully interrupt signal processor realizes now the fir is ready to start the calculation with the data we buffered in DMA. When the calculation is finished and the calculated data was written in the buffers, the out full interrupt is set for interrupting PUNEH to save the data in the ram. After finishing this operation out\_complete interrupts PUNEH to clear the configuration registers of DMA.


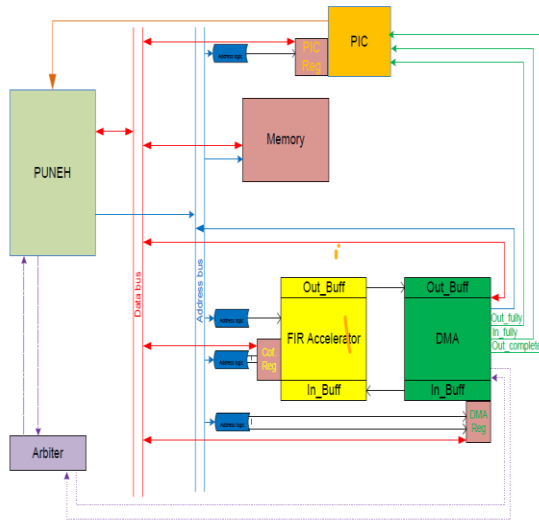


Figure 1


In the next parts, the design of the components will be described and illustrated for realizing their operations.
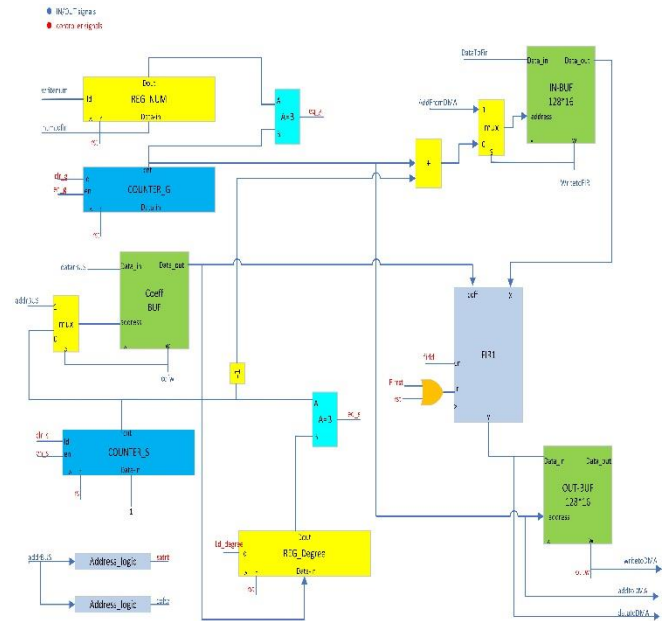
## B. FIR

for this FIR filter, I use a 1 level fir filter consequentially to Degree, IN-BUF, OUT-BUFF, and other parts to reach our goal. the overview of our design and the main signal are illustrated here:



 AND the controller for this DATA PATH is shown below:



And the top module of this fir has this ports:

```
ENTITY FIR_TOP IS PORT (
    clk : IN STD_LOGIC;
    r : IN STD_LOGIC;
    databus : IN STD_LOGIC_VECTOR(15 DOWNTO 0);
    addbus : IN STD_LOGIC_VECTOR(15 DOWNTO 0);
    --to DMA
    DataToFir : IN STD_LOGIC_VECTOR(15 DOWNTO 0);
    NUMToFir : IN STD_LOGIC_VECTOR(15 DOWNTO 0);
    AddFromDMA : IN STD_LOGIC_VECTOR(6 DOWNTO 0);
    writeNUM, writetoFIR : IN STD_LOGIC;
    WriteToDMA : OUT STD_LOGIC;
    DataToDMA : OUT std_logic_vector(15 DOWNTO 0);
    AddToDMA : OUT std_logic_vector(6 DOWNTO 0);
    FirComplete : OUT STD_LOGIC
);
END ENTITY FIR_TOP;
```

### C. PIC


a programmable interrupt controller (PIC) is an integrated circuit that helps a microprocessor (or CPU) handle interrupt requests (IRQ) coming from multiple different sources (like external I/O devices) which may occur simultaneously.[1] It helps prioritize IRQs so that the CPU switches execution to the most appropriate interrupt handler (ISR) after the PIC assesses the IRQ's relative priorities.

PIC must activate the interrupt of PUNEH and give the isr address of the related interrupt. The codes are shown below:


```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3  USE IEEE.numeric_std.all;
4
5  ENTITY PIC IS
6  GENERIC (
7      ADDR1SR : STD_LOGIC_VECTOR(15 DOWNTO 0) := x"0C05";
8      IR1ISR : STD_LOGIC_VECTOR(15 DOWNTO 0) := x"0900";
9      IR2ISR : STD_LOGIC_VECTOR(15 DOWNTO 0) := x"0910";
10     IR3ISR : STD_LOGIC_VECTOR(15 DOWNTO 0) := x"0920"
11 );
12 PORT(
13     IR1,IR2,IR3 :IN STD_LOGIC;
14     ADDRBUS :IN STD_LOGIC_VECTOR(15 DOWNTO 0);
15     DATABUS :OUT STD_LOGIC_VECTOR(15 DOWNTO 0);
16     INT :OUT STD_LOGIC
17 );
18 END ENTITY;
19
20 ARCHITECTURE ARCH OF PIC IS
21 TYPE MEMORY IS ARRAY(NATURAL RANGE<>) OF STD_LOGIC_VECTOR(15 DOWNTO 0);
22 SIGNAL MEM:MEMORY(2 DOWNTO 0) := (IR3ISR,IR2ISR,IR1ISR);
23 BEGIN
24     INT<='1' WHEN ((IR1 OR IR2 OR IR3)='1') ELSE '0';
25     DATABUS<= MEM(0) WHEN (IR1='1' AND ADDRBUS=ADDRLOGIC) ELSE MEM(1) WHEN (IR2='1' AND ADDRBUS=ADDRLOGIC)
26     ELSE MEM(2) WHEN (IR3='1' AND ADDRBUS=ADDRLOGIC) ELSE (OTHERS=>'Z');
27 END ARCHITECTURE;

```

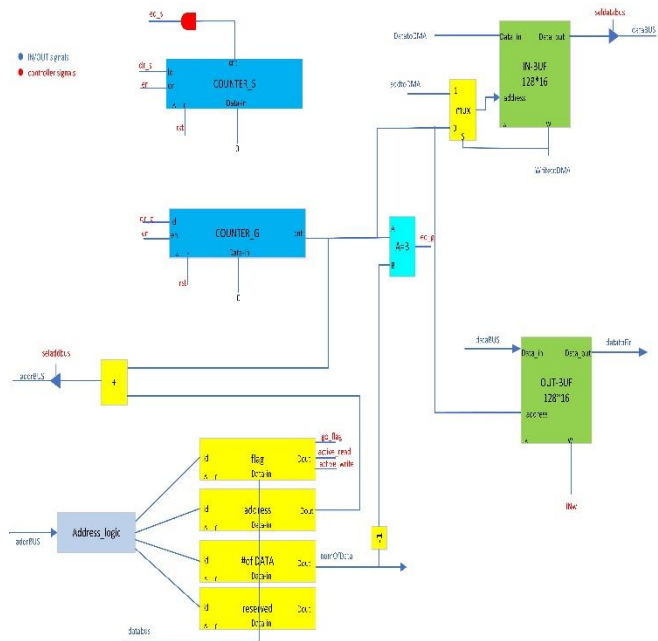

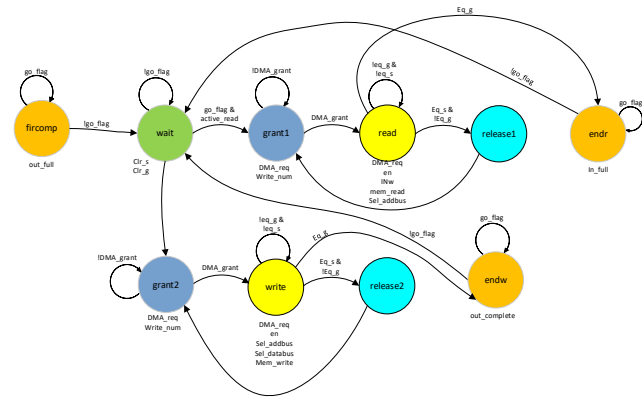Also the controller of this is like below:



### D. DMA

DMA Controller is a hardware device that allows I/O devices to directly access memory with less participation of the processor. when the CPU is using programmed input/output, it is typically fully occupied for the entire duration of the read or write operation and is thus unavailable to perform other work. With DMA, the CPU first initiates the transfer, then it does other operations while the transfer is in progress, and it finally receives an interrupt from the DMA controller when the operation is done. This feature is useful at any time that the CPU cannot keep up with the rate of data transfer, or when the CPU needs to perform work while waiting for a relatively slow I/O data transfer. Our DMA read and writes in burst mode.

The Data path of my DMA is illustrated below:

And the top module of this DMA has this ports:

```


▼ ENTITY DMA_TOP IS
  PORT (
    clk ,rst : IN std_logic;
    DMA_grant : IN std_logic;
    writetoDMA : IN std_logic;
    datatoDMA : IN std_logic_vector(15 downto 0);
    addrtoDMA : IN std_logic_vector(6 downto 0);
    firComplete : IN std_logic;
    addrbus : INOUT std_logic_vector(15 downto 0);
    databus : INOUT std_logic_vector(15 downto 0);
    writetoFIR : OUT std_logic;
    DMA_req : OUT std_logic;
    out_full : OUT std_logic;
    in_full : OUT std_logic;
    datatoFIR : OUT std_logic_vector(15 downto 0);
    cnt_g : OUT std_logic_vector(6 DOWNTO 0);
    write_num : OUT std_logic;
    mem_read : OUT std_logic;
    mem_write : OUT std_logic;
    numOfData : OUT std_logic_vector(15 downto 0);
    out_complete : OUT std_logic
  );
END ENTITY DMA_TOP;

```

## E.ARBITTER

the bus arbiter is a device used in a multi-master bus system to decide which bus master will be allowed to control the bus for each bus cycle.

Basic Arbiter

 

Requests			Grants		
R1	R2	R3	G1	G2	G3
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0


The content of the code parts is :

00000	1A00
00001	3B00
00002	1A01
00003	3B01
00004	1A02
00005	3B02
00006	1A03
00007	3B03
00008	1A04
00009	3B04
0000a	1A05
0000b	3B05
0000c	1A06
0000d	3B06
0000e	1A07
0000f	3B07
00010	1A08
00011	3B08
00012	1A09
00013	3B09
00014	1A0A
00015	3B0A
00016	1A0B
00017	3B0B
00018	1A0C
00019	3B0C
0001a	1A0D
0001b	3B0D
0001c	1A0E
0001d	3B0E
0001e	1A0F
0001f	3B0F
00020	1A10
00021	3C01
00022	1A11
00023	3C02
00024	1A12
00025	3C00
00026	0000
00027	0000
00028	0000
00029	0000

Until 1f the coefficients registers will be filled and from 20 to 25 the DMA registers will be set for reading the data and filling them in the fir input buffer.
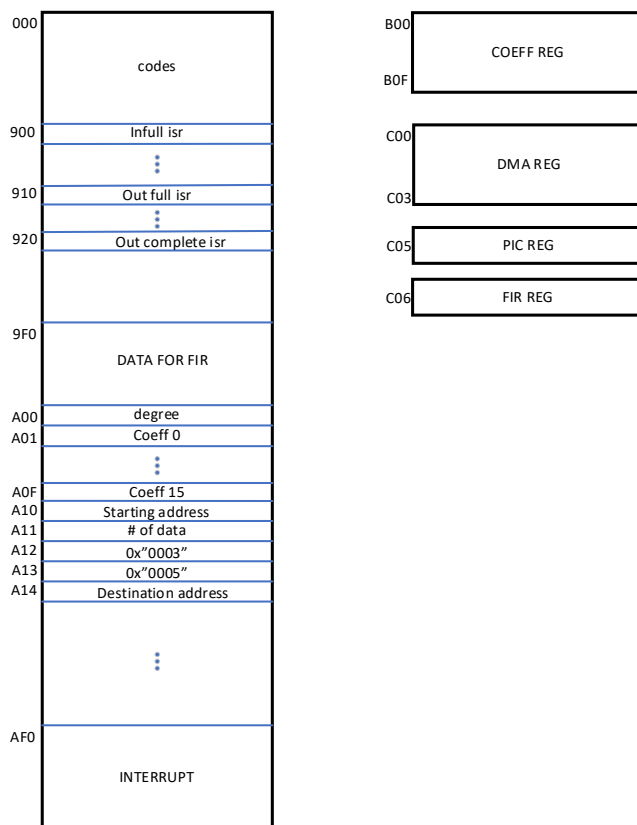
## E.MEMORY MAP ADDRESS

The addresses which I set for testing my work are like this :



--And the contents of interrupt is :

AF0: PC  
 AF1: SIC(FC)  
 AF2: JMN(C05)  
 AF3: RIC  
 AF4: EIN  
 AF5: JMN(AF0)  
 .  
 .  
 .  
 AFC: AC  
 AFD: OF  
 AFE: IN  
 AFF: SR

--And the contents of infull isr is :

900: STA(C06)  
 901: ACZ  
 902: STA(C00)  
 903: JMA(AF3)

--And the contents of out full isr is :

910: LDA(A14)  
 911: STA(C01)  
 912: LDA(A13)  
 913: STA(C00)  
 914: JMA(AF3)

--And the contents of out complete isr is :

920: ACZ  
 921: STA(C00)  
 922: JMA(AF3)

--The destination address is A15

0a14 |0A15

--# of data is 8

00a11 |0008

--starting address is 9F0

00a10 |09F0

--the degree is 3 and coefficients are :

0a00 |0003  
 0a01 |0001  
 0a02 |0001  
 0a03 |0002  
 0a04 |0003  
 0a05 |0004  
 0a06 |0005  
 0a07 |0006  
 0a08 |0007  
 0a09 |0008  
 0a0a |0009  
 0a0b |000A  
 0a0c |000B  
 0a0d |000C  
 0a0e |000D  
 0a0f |000E

--the input data for calculation is :


09f0 |0000  
 09f1 |0001  
 09f2 |0002  
 09f3 |0003  
 09f4 |0004  
 09f5 |0005  
 09f6 |0006  
 09f7 |0007  
 09f8 |0008  
 09f9 |0009  
 09fa |000A  
 09fb |000B  
 09fc |000C  
 09fd |000D  
 09fe |000E  
 09ff |000F

Because the number of data is 8 we just use 0,1,2,3,4,5,6,7.

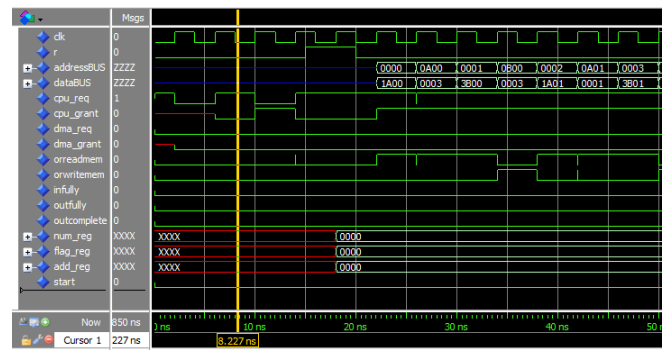
## F.TESTING

For the verification of this code, according to the memory contents of the previous part, a test bench was made(TB) which proves the authenticity of our design.

Now we can see After resetting the system the arbiter gives permission the CPU to get the bus and run the codes:



 
After running the codes until the address 1F, we fill the FIR coefficient ram with the data in memory from A00 to A0F:






Memory Data - /test\_fir/test/fir\_inst/DP/RAM\_coeff/mem

File	Edit	View	Bookmarks	Window	Help
Memory Data - /test_fir/test/fir_inst/DP/RAM_coeff/mem - Default					
Goto: <input type="text"/>					
0	0003				
1	0001				
2	0001				
3	0002				
4	0003				
5	0004				
6	0005				
7	0006				
8	0007				
9	0008				
10	0009				
11	000A				
12	000B				
13	000C				
14	000D				
15	000E				

 
with running the codes from 20 to 25 the registers of DMA will be set :



 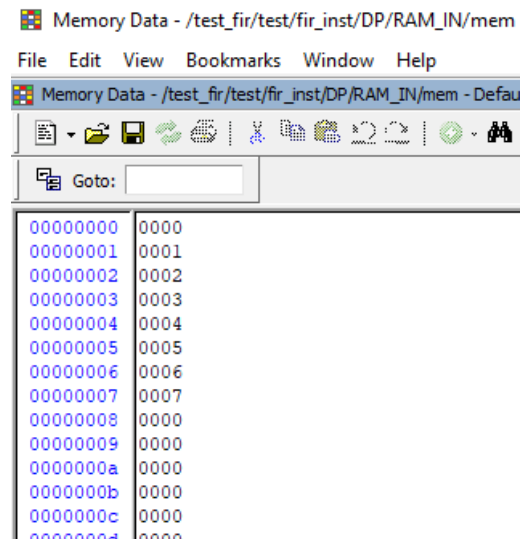 
Now the DMA wants to start reading from memory so get the bus and write the data in the input buffer of DMA and FIR, after this the DMA set the in full interrupt :



 Now the CPU goes to the interrupt part and run the in full isr codes. Start of fir will set here:



 When the fir completes its job and puts the calculated data in out buffer of DMA, the DMA set the out full interrupt and out full isr will be run:



You can see the calculated data of fir in out buffer of DMA. Remind that the number if our data is 8 and the degree is 3 so the data from 0 to 5 are valid and others are invalid:

